

Name, Surname :
 Number :
 Course Code :
 Course Name :
 Exam : Quiz Midterm Final
 Date :


Please make sure to write your name and student number on each paper that you have used

Question Number	1	2	3	4	5	Total
Mark						

Note: Exam duration is 60 minutes only.

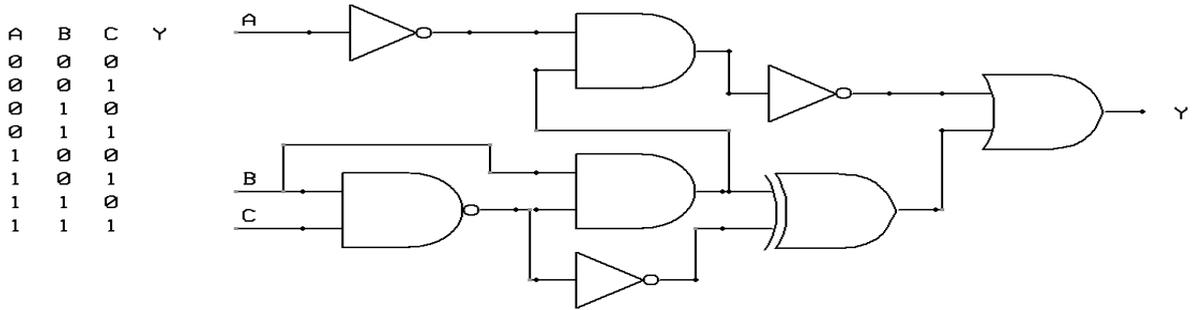Questions

1- Determine the Boolean function for output **Y** as a functions of three input A,B,C in figure below



- 2- Design a combinational circuits that subtract **one to a 4 bit binary number**, A_3, A_2, A_1, A_0 . For example, if the input of the circuit is, $A_3, A_2, A_1, A_0 = 1101$, the output is $1101 - 1 = 1100$
- 3- **Simplify** the boolean function, $F(a,b,c,d) = \sum(1,3,6,9,11,15)$, don't care conditions $d(a,b,c,d) = \sum(4,5,7,10,12)$ and **draw** the logic circuit.
- 4- Design a combinational circuit with **three inputs** and **one output**. The output is 1 when the binary value of the inputs is less than 3. The output is 0 otherwise.
- 5- Design the 3 bit full adder with using **3x8 decoder** and **OR gates**